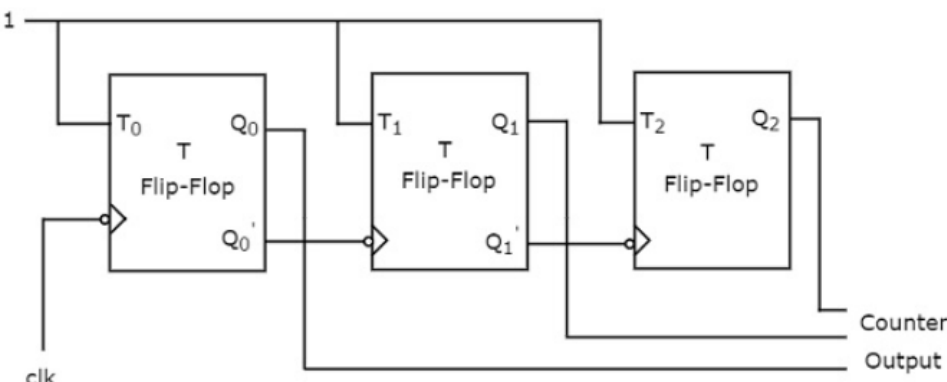


Q.4	Solve Any Two of the following.		12
A)	Compare Characteristics of TTL, CMOS, ECL, RTL, I ² L and DCTL logic families.	(3)	6
B)	Define and explain: i) Fan in and Fan out ii) Noise immunity iii) Propagation Delay	(1,2)	6
C)	Explain in brief the operation of CMOS NAND Gate with schematic diagram.	(3)	6
Q. 5	Solve Any Two of the following.		12
A)	Implement given Boolean functions using PLA, PAL and PROM F ₁ (A,B,C)= $\sum m(0, 2,6,7)$ F ₂ (A,B,C)= $\sum m(1, 3,4,5,7)$	(4)	6
B)	Write VHDL code for Mux 4:1 using dataflow and behavioural architecture style.	(4)	6
C)	Classify memories RAM and ROM.	(3)	6
	*** End ***		

The grid and the borders of the table will be hidden before final printing.

Instructions to the Students:


1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

	(Level/CO)	Marks
Q. 1 Solve Any Two of the following.		12
A) Convert the following Boolean equation into standard SOP and POS form. $F(A,B,C) = AB + AC' + BC$	L2	6
B) Write VHDL code for full adder using Structural architecture method.	L3	6
C) Explain TTL logic in detail.	L2	6
Q.2 Solve Any Two of the following.		12
A) Draw the counter output of the following sequential circuit using clock diagram.	L2	6
		
B) What is the difference between TTL and CMOS and ECL?	L2	6
C) Explain General Architecture of CPLD in detail.	L2	6
Q. 3 Solve Any Two of the following.		12
A) Draw the Moore state diagram for One bit Serial adder.	L2	6
B) Implement the following Boolean functions using PAL and PROM. $A(X,Y,Z) = \sum m(4,6,7)$, $B(X,Y,Z) = \sum m(2, 4, 5,6)$	L3	6

- C) Minimise the following function in SOP and POS form using K-Maps: **L3 6**
- $F(A, B, C, D) = m(1, 2, 6, 7, 8, 13, 14, 15) + d(0, 3, 5, 12)$

Q.4 Solve Any Two of the following. **12**

 - A) Explain the universal shift register operation with diagram. **L3 6**
- B) The logic function is implemented by the multiplexer circuit is **L3 6**
 (“ground implies a logic 0”) find the output of F?



- C) Write VHDL code for 4-bit up counter. **L3 6**

Q. 5 Solve Any Two of the following. **12**

- A) Implement the following function using **L3 6**
 i) multiplexer 8x1 ii) multiplexer 2x1
 $F(A,B,C,D) = m(0,1,3,5,7,10,11,14)$
- B) Design sequence detector to detect three or more consecutive 1's in **L3 6**
 string of bits coming through an input lines.
- C) i) What is disadvantage in SR flipflop? **L2 6**
 ii) What is difference between T flipflop and D flipflop?
 iii) Write down the next state equation of T flipflop.

***** End *****

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE

Regular & Supplementary Winter Examination – 2023

Course: B. Tech. Branch: Electronics/Electronics & telecom/Electronics & comm

Semester: III

Subject Code & Name: (BTEXC303/BTETC303) Digital Electronics

Max Marks: 60

Date:06/01/2024

Duration: 3 Hrs.

Instructions to the Students:

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

	Level/(CO)	Marks
Q. 1 Solve Any Two of the following.		12
A) Minimize the following Boolean function using K-map $F(A, B, C, D) = \sum m(0, 1, 2, 3, 8, 9, 11, 14) + d(5, 6, 7, 13)$	CO1	6
B) Implement 5:32 decoder using 3:8 decoder	CO2	6
C) Convert the following Boolean expression given below in both standard SOP and standard POS forms: $F = (X + Y')(X + Z)$	CO1	6
Q.2 Solve Any Two of the following.		12
A) i) On the third clock pulse, a 4-bit Johnson sequence is $Q_0 = 1, Q_1 = 1, Q_2 = 1$, and $Q_3 = 0$. On the fourth clock pulse, the sequence is _____. ii) Draw the 4-bit Johnson counter using D flip flop.	CO2	6
B) Explain SR, JK, T, D flip flop in detail & write next state equation.	CO2	6
C) Design 4 bit serial-in-parallel -out shift register is initially set to 1111. Data 1010 is applied as the input. What will be the output after 3 clock pulses?	CO1	6
Q. 3 Solve Any Two of the following.		12
A) Draw the mealy state diagram for sequence detector 1010.	CO4	6
B) Draw state diagram of JK flip flop?	CO2	6
C) Design 8:1 MUX using a) 4:1 MUX. Tree b) Only one 2:1 MUX	CO2	6
Q.4 Solve Any Two of the following.		12
A) Define the following term a) Propagation delay b) Fanout c) Power Dissipation d) Figure of Merit	CO2	6

- | | | |
|---|-----|---|
| B) Draw the CMOS schematic and stick diagram for NAND gate. | CO3 | 6 |
| C) Explain CMOS inverter characteristics using cutoff, active and saturation regions of operations. | CO4 | 6 |

Q. 5 Solve Any Two of the following. 12

- | | | |
|---|-----|---|
| A) Explain General Architecture of FPGA in detail. | CO2 | 6 |
| B) Implement the following Boolean function using PAL, PLA
$F1 = \sum m(3,5,7)$ and $F2 = \sum m(4,5,7)$. | CO3 | 6 |
| C) Write VHDL code for full adder using structural style. | CO4 | 6 |

***** End *****

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE

Supplementary Examination Summer 2024

Course: B. Tech. Branch : E&TC / Electronics & Comm. / Electronics Engineering Semester : III

Subject Code & Name: BTETC303 / BTEXC303 Digital Electronics

Max Marks: 60

Date: 04/07/2024

Duration: 3 Hr.

Instructions to the Students:

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

(Level) Marks

Q.1 Solve Any Two of the following. 12

- A) Design a full-adder circuit and provide the truth table, logic diagram, and simplified logic expressions for the sum and carry outputs. Level 2 6
- B) Design a BCD-to-7 segment decoder and provide the truth table for each segment output (a, b, c, d, e, f, g). Level 1 6
- C) Implement the following functions using Multiplexers. Level 4 6
 $F(A,B,C,D) = \sum m(0,1,3,4,8,9,15)$

Q.2 Solve Any Two of the following. 12

- A) Simplify the following logic function using a K-map and express the simplified form in both SOP and POS: $F(A,B,C,D) = \sum m(0,2,5,7,8,10,13,15)$ Level 4 6
- B) What is a clocked SR flip-flop? Explain its operation with the help of a truth table and logic diagram. Level 4 6
- C) Describe how a T flip-flop can be derived from a JK flip-flop. Level 3 6

Q.3 Solve Any Two of the following. 12

- A) What is shift register? Explain its working with the help of a diagram & truth table. Level 1 6
- B) Distinguish between Mealy and Moore machines in terms of their design and applications. Level 5 6
- C) Design a finite state machine to detect the sequence "1101" using D flip-flops. Level 4 6

Q.4 Solve Any Two of the following. 12

- A) Briefly explain any six characteristics of Digital ICs. Level 1 6
- B) Describe the construction and operation of CMOS NAND and NOR gates. Level 2 6
- C) Discuss the advantages and disadvantages of using CMOS over TTL in modern digital circuits. Level 3 6

- Q. 5 Solve Any Two of the following.** **12**
- A) Describe the architecture and operation of a Programmable Logic Array (PLA). *Level 2* **6**
How does it differ from a PAL?
- B) Distinguish between SRAM and DRAM *Level 3* **6**
- C) Write a VHDL code for a full adder using structural description. *Level 2* **6**

***** End *****