

**DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE**

**Regular End Semester Examination – Summer 2022**

**Course: B. Tech.**

**Branch : Electrical**

**Semester :VI**

**Subject Code & Name: BTEEC603 POWER ELECTRONICS**

**Max Marks: 60**

**Date:26/08/022**

**Duration: 3.45 Hr.**

**Instructions to the Students:**

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in ( ) in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

(Level/CO) Marks

**Q. 1 Solve Any Two of the following.**

- |  |             |          |
|--|-------------|----------|
| A) Explain V-I characteristics of Power Diode.                 | <b>CO-2</b> | <b>6</b> |
| B) Give the Advantages, disadvantages and application of IGBT. | <b>CO-3</b> | <b>6</b> |
| C) Explain V-I characteristics of SCR.                         | <b>CO-2</b> | <b>6</b> |

**Q.2 Solve Any Two of the following.**

- |   |             |          |
|---|-------------|----------|
| A) Give comparison between R triggering, RC triggering, UJT triggering. | <b>CO-2</b> | <b>6</b> |
| B) Explain Commutation.   | <b>CO-2</b> | <b>6</b> |
| C) Explain Thyristor Firing Circuit.                                    | <b>CO-3</b> | <b>6</b> |

**Q. 3 Solve Any Two of the following.**

- |   |             |          |
|---|-------------|----------|
| A) Explain effect of source inductance on the performance of 3 phase Full bridge diode rectifier. | <b>CO-2</b> | <b>6</b> |
| B) Explain 1 phase Half wave rectifier with R-L Load and freewheeling diode.                      | <b>CO-2</b> | <b>6</b> |
| C) Explain 1 $\phi$ Half wave diode Rectifier with R Load.  | <b>CO-2</b> | <b>6</b> |

**Q.4 Solve Any Two of the following.**

- |   |             |          |
|---|-------------|----------|
| A) Explain single phase Full wave AC voltage controller with RL Load. | <b>CO-2</b> | <b>6</b> |
| B) Explain single phase half wave AC Voltage controller with R-Load.  | <b>CO-2</b> | <b>6</b> |
| C) Compare ON-OFF Control and Phase angle control.                    | <b>CO-3</b> | <b>6</b> |

**Q. 5 Solve Any Two of the following.**

- |   |             |          |
|---|-------------|----------|
| A) Explain principle of Step-down chopper (Back) operation. | <b>CO-2</b> | <b>6</b> |
| B) Explain performance parameters of Inverter.              | <b>CO-2</b> | <b>6</b> |
| C) Explain half bridge inverter with R-load.                | <b>CO-2</b> | <b>6</b> |

**\*\*\* End \*\*\***